


Counters, Shift Registers & Memories

Design the following circuits using Verilog **and create a testbench** for each design to check its functionality

1) Implement the following Parameterized Shift register

- Parameters

Name	Value	Description
LOAD_AVALUE	Integer > 0	Value loaded with aset is high
SHIFT_DIRECTION	"LEFT" or "RIGHT"	Direction of the shift register. Default = "LEFT"
LOAD_SVALUE	Integer > 0	Value loaded with sset is high with the rising clock edge
SHIFT_WIDTH	Integer > 0	Width of data[] and q[] ports

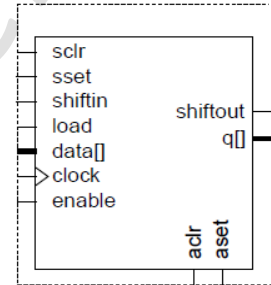

- Ports

Name	Type	Description
sclr	Input	Synchronous clear input. If both sclr and sset are asserted, sclr is dominant.
sset		Synchronous set input that sets q[] output with the value specified by LOAD_SVALUE. If both sclr and sset are asserted, sclr is dominant.
shiftin		Serial shift data input
load		Synchronous parallel load. High: Load operation with data[], Low: Shift operation
data[]		Data input to the shift register. This port is SHIFT_WIDTH wide
clock		Clock Input
enable		Clock enable input
aclr		Asynchronous clear input. If both aclr and aset are asserted, aclr is dominant.
aset	Output	Asynchronous set input that sets q[] output with the value specified by LOAD_AVALUE. If both aclr and aset are asserted, aclr is dominant.
shiftout		Serial Shift data output
q[]		Data output from the shift register. This port is SHIFT_WIDTH wide

- Note that the synchronous control signals "sclr and sset" have dominance over the enable signal but the enable signal is dominant over the load signal.

2)

1. Implement Asynchronous D Flip-Flop with Active low reset

Inputs: d, rstn, clk


Outputs: q, qbar

2. Implement 4-bit Ripple counter with asynchronous active low set using behavioral modelling that increment from 0 to 15
3. Implement the below 4-bit Ripple counter using structural modelling (Instantiate DFF previously designed in step 1). Ripple counter output "out" is connected to qn0, qn1, qn2, qn3 which are connected to the qn output of each DFF as shown below)

Inputs: clk, rstn

Outputs: [3:0] out

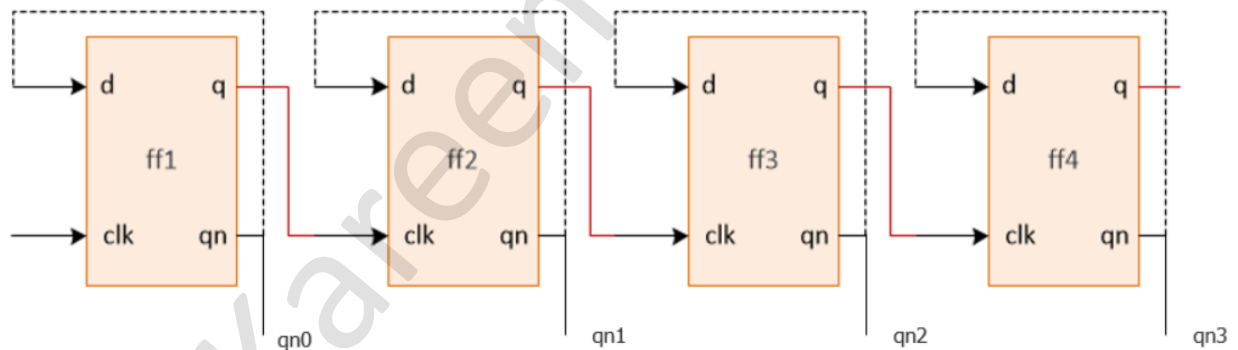4. Test the above structural design using a testbench
 - Testbench should instantiate the previous two counters designed in steps 2 and 3
 - Consider the behavioral design as the golden model and check the functionality of the structural design




3) Implement the following single port synchronous write/read

- Parameters

Name	Description	Default values
MEM_WIDTH	Data in/out and memory word width	16
MEM_DEPTH	Memory depth	1024
ADDR_SIZE	Address size based upon the memory depth	10
ADDR_PIPELINE	If "TRUE" then the address should be pipelined before writing/reading the RAM, if "FALSE" then the address input will be assigned directly to the RAM's address port	FALSE
DOUT_PIPELINE	If "TRUE" then the data out should be pipelined, if "FALSE" then the output will be out of the RAM directly	TRUE
PARITY_ENABLE	If the parameter value is 1 then the parity should be calculated and assigned to parity_out port, if the parameter is 0 then the parity_out port should be tied to 0	1

- Added ports functionality

 - addr_en: enable signal for the flipflop that pipelines the address
- dout_en: enable signal for the flipflop that pipelines the data out
- parity_out: calculates the parity on the dout bus



Extra Problems to be solved:

Implement N-bit parameterized Full/Half adder

- Parameters
 - WIDTH: Determine the width of input a,b, sum
 - PIPELINE_ENABLE: if this parameter is high then the output of the sum and carry will be pipelined otherwise the circuit is pure combinational, default is high
 - USE_FULL_ADDER: if this parameter is high then cin signal will be used during the cout and sum calculation from the input signals, otherwise if this parameter is low ignore the cin input, default is high
- Ports

Name	Type	Description
a	Input	Data input a of width determined by WIDTH parameter
b		Data input b of width determined by WIDTH parameter
clk		Clk input
cin		Carry in bit
rst		Active high synchronous reset
sum	Output	sum of a and b input of width determined by WIDTH parameter
cout		Carry out bit
parity_out		Parity bit that should be 1 if the if the number of 1's in the sum and cout is odd (instantiate the parity module inside the full adder)